

Problems for Assignment 3

(All problems must be done in dsch2 and you can't use a pre designed gate. You need to build the gate from scratch)

1. Derive the Boolean logic expression from the following K-Map and implement the logic function using CMOS technology. You may use blocks/sub-circuits made using CMOS technology but cannot use readily available logic gates.

CD \ AB				
	00	01	11	10
00	1	0	1	1
01	1	d	d	0
11	d	d	1	0
10	1	1	0	1

Expected Output:

Show the necessary steps to derive the logic expression from the K-Map and draw the CMOS circuit in dsch2. Assign clocks of suitable frequencies to each of the inputs so that all possible input combinations are generated in the timing diagram. From your timing diagram explain one case where *Output* = 1 and another case where *Output* = 0. Verify the values with your theoretical values calculated from the logic expressions.

2. Implement the following logic expression using an **16 to 1** multiplexer.

$$f(A,B,C,D,E) = \sum(0,4,5,8,9,12,15,21,22,29,30); \text{ don't care } 7$$

The **16 to 1** multiplexer is to be designed using sub-circuit blocks of **4 to 1** multiplexers only.